


# Microwave Filter Design

## Chp3. Basic Concept and Theories of Filters

Prof. Tzong-Lin Wu

Department of Electrical Engineering  
National Taiwan University

Prof. T. L. Wu

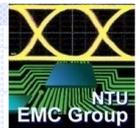

## Transfer Functions

### General Definitions

- Transfer function: a mathematical description of network response characteristics.
- The transfer function of a 2-port filter network is usually defined as:

$$|S_{21}(j\Omega)|^2 = \frac{1}{1 + \varepsilon^2 F_n^2(\Omega)}$$

where  $\varepsilon$  is the *ripple constant*,  $F_n(\Omega)$  is the *characteristic function*, and  $\Omega$  is the *frequency variable* of a lowpass prototype filter that has a cutoff frequency  $\Omega = \Omega_c$  for  $\Omega_c = 1$  (rad/s).

- For linear, time invariant networks, the transfer function may be defined as a rational function:

$$S_{21}(p) = \frac{N(p)}{D(p)}$$

where  $N(p)$  and  $D(p)$  are polynomials in a complex frequency variable  $p = \sigma + j\Omega$ . For a lossless passive network, the neper frequency (damping coefficient)  $\sigma = 0$  and  $p = j\Omega$ .

Prof. T. L. Wu

# Transfer Functions: Definitions

## Insertion Loss

$$L_A(\Omega) = 10 \log \frac{1}{|S_{21}(j\Omega)|^2} \text{ dB}$$

## Return Loss

$|S_{11}|^2 + |S_{21}|^2 = 1$  for a lossless, passive two-port network,

$$L_R(\Omega) = 10 \log[1 - |S_{21}(j\Omega)|^2] \text{ dB}$$

## Phase Response

$$\phi_{21} = \text{Arg } S_{21}(j\Omega)$$

## Group Delay Response

$$\tau_d(\Omega) = \frac{d\phi_{21}(\Omega)}{-d\Omega} \text{ seconds}$$

Prof. T. L. Wu

# Transfer Functions: Poles and Zeros on the Complex Plane

Complex Plane ( $p$ -plane) :  $(\sigma, \Omega)$

The values of  $p$  at which the function becomes zero are the zeros of the function, and the values of  $p$  at which the function becomes infinite are the singularities (usually the poles) of the function.

Therefore, the zeros of  $S_{21}(p)$  are the roots of the numerator  $N(p)$  and the poles of  $S_{21}(p)$  are the roots of denominator  $D(p)$ .

These poles will be the natural frequencies of the filter.

For the filter to be stable, these natural frequencies must lie in the left half of the  $p$ -plane, or on the imaginary axis.

$D(p)$  is a Hurwitz polynomial, i.e., its roots (or zeros) are in the inside of the left half-plane, or on the  $j$ -axis,

the roots (or zeros) of  $N(p)$  may occur anywhere on the entire complex plane. The zeros of  $N(p)$  are called finite-frequency transmission zeros of the filter.

Prof. T. L. Wu

## Butterworth (Maximally Flat) Response


The amplitude-squared transfer function for Butterworth filters that have an insertion loss  $L_{Ar} = 3.01$  dB at the cutoff frequency  $\Omega_c = 1$  is given by

$$|S_{21}(j\Omega)|^2 = \frac{1}{1 + \Omega^{2n}}$$

where  $n$  is the degree or the order of filter, which corresponds to the number of reactive elements required in the lowpass prototype filter.

**Maximally flat** because its amplitude-squared transfer function has the maximum number of  $(2n - 1)$  zero derivatives at  $\Omega = 0$ .

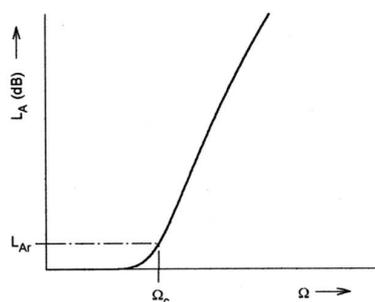Therefore, the maximally flat approximation to the ideal lowpass filter in the pass-band is best at  $\Omega = 0$ , but **deteriorates as  $\Omega$  approaches the cutoff frequency  $\Omega_c$** . Fig-





Prof. T. L. Wu

## Butterworth (Maximally Flat) Response

A **rational transfer function** constructed from (3.7) is


$$S_{21}(p) = \frac{1}{\prod_{i=1}^n (p - p_i)} \quad p_i = j \exp \left[ \frac{(2i - 1)\pi}{2n} \right]$$

There is **no finite-frequency transmission zero** [all the zeros of  $S_{21}(p)$  are at infinity], and the poles  $p_i$  lie on the **unit circle** in the **left half-plane** at equal angular spacings, since  $|p_i| = 1$  and  $\text{Arg } p_i = (2i - 1)\pi/2n$ . This is illustrated in Figure 3.2.

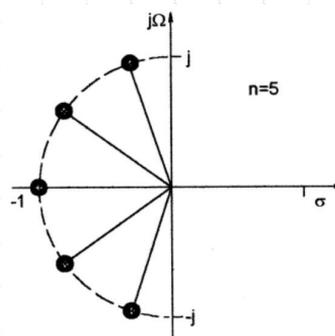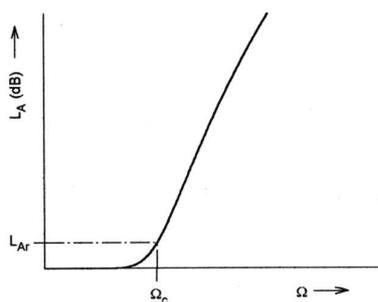

rof. T. L. Wu

## Order dependence

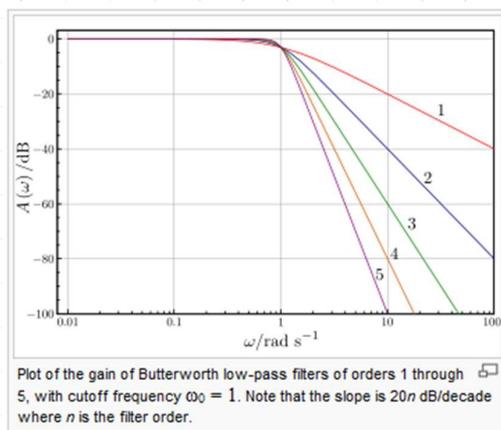

Prof. T. L. Wu

## Chebyshev Response

The Chebyshev response that exhibits the **equal-ripple passband** and **maximally flat stopband** is depicted in Figure 3.3. The amplitude-squared transfer function that describes this type of response is

$$|S_{21}(j\Omega)|^2 = \frac{1}{1 + \varepsilon^2 T_n^2(\Omega)} \quad (3.9)$$

where the ripple constant  $\varepsilon$  is related to a given passband ripple  $L_{Ar}$  in dB by

$$\varepsilon = \sqrt{10^{\frac{L_{Ar}}{10}} - 1} \quad (3.10)$$

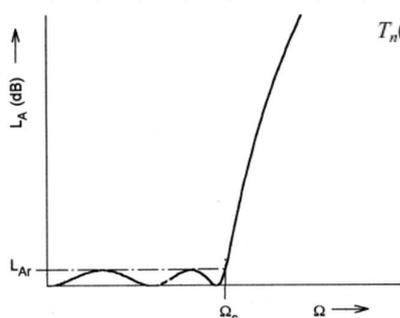


FIGURE 3.3 Chebyshev lowpass response.

$T_n(\Omega)$  is a Chebyshev function of the first kind of order  $n$ , which is defined

$$T_n(\Omega) = \begin{cases} \cos(n \cos^{-1} \Omega) & |\Omega| \leq 1 \\ \cosh(n \cosh^{-1} \Omega) & |\Omega| \geq 1 \end{cases}$$

Prof. T. L. Wu

## Chebyshev Polynomial

Chebyshev Differential Equations

$$(1 - x^2) y'' - x y' + n^2 y = 0$$

$$(1 - x^2) y'' - 3x y' + n(n + 2) y = 0$$

The solutions are the Chebyshev polynomials of the first and second kind, respectively

Chebyshev Polynomial of the first kind

$$T_0(x) = 1$$

$$T_1(x) = x$$

$$T_{n+1}(x) = 2xT_n(x) - T_{n-1}(x)$$

The Chebyshev polynomials of the first kind can be defined by the trigonometric identity

$$T_n(x) = \cos(n \arccos x) = \cosh(n \operatorname{arccosh} x)$$

$$\rightarrow T_n(\cos(\vartheta)) = \cos(n\vartheta)$$

Chebyshev Polynomial of the second kind

$$U_0(x) = 1$$

$$U_1(x) = 2x$$

$$U_{n+1}(x) = 2xU_n(x) - U_{n-1}(x).$$

The Chebyshev polynomials of the second kind can be defined by the trigonometric identity

$$U_n(\cos(\vartheta)) = \frac{\sin((n+1)\vartheta)}{\sin \vartheta}$$

Prof. T. L. Wu

## Chebyshev Response

Rhodes has derived a general formula of the rational transfer function

$$S_{21}(p) = \frac{\prod_{i=1}^n [\eta^2 + \sin^2(i\pi/n)]^{1/2}}{\prod_{i=1}^n (p + p_i)}$$

$$p_i = j \cos \left[ \sin^{-1} j\eta + \frac{(2i-1)\pi}{2n} \right]$$

$$\eta = \sinh \left( \frac{1}{n} \sinh^{-1} \frac{1}{\varepsilon} \right)$$

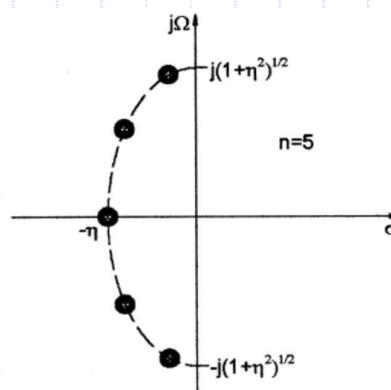


FIGURE 3.4 Pole distribution for Chebyshev response.

Similar to the maximally flat case, all the transmission zeros of  $S_{21}(p)$  are located at infinity. Therefore, the Butterworth and Chebyshev filters dealt with so far are sometimes referred to as all-pole filters.

The pole locations for the Chebyshev lie on an ellipse in the left half-plane.

Prof. T. L. Wu

## Poles of Chebyshev Filter

Using the complex frequency  $s$ , the poles satisfy

$$1 + \varepsilon^2 T_n^2(-js) = 0$$

Defining  $-js = \cos(\theta)$  and using the trigonometric definition of the Chebyshev polynomials yields

$$1 + \varepsilon^2 T_n^2(\cos(\theta)) = 1 + \varepsilon^2 \cos^2(n\theta) = 0.$$

Solving for  $\theta$

$$\theta = \frac{1}{n} \arccos\left(\frac{\pm j}{\varepsilon}\right) + \frac{m\pi}{n}$$

The poles of the Chebyshev gain function are then

$$\begin{aligned} s_{pm} &= j \cos(\theta) \\ &= j \cos\left(\frac{1}{n} \arccos\left(\frac{\pm j}{\varepsilon}\right) + \frac{m\pi}{n}\right) \end{aligned}$$


Using the properties of the trigonometric and hyperbolic functions, this may be written in explicitly complex form:

$$\begin{aligned} s_{pm}^{\pm} &= \pm \sinh\left(\frac{1}{n} \operatorname{arsinh}\left(\frac{1}{\varepsilon}\right)\right) \sin(\theta_m) & \text{where } m = 1, 2, \dots, n \text{ and} \\ &+ j \cosh\left(\frac{1}{n} \operatorname{arsinh}\left(\frac{1}{\varepsilon}\right)\right) \cos(\theta_m) & \theta_m = \frac{\pi}{2} \frac{2m-1}{n} \end{aligned}$$

It demonstrates that the poles lie on an **ellipse** in  $s$ -space centered at  $s = 0$  with a real semi-axis of length  $\sinh(\operatorname{arsinh}(1/\varepsilon)/n)$  and an imaginary semi-axis of length of  $\cosh(\operatorname{arsinh}(1/\varepsilon)/n)$

Prof. T. L. Wu

## Poles of Chebyshev Filter

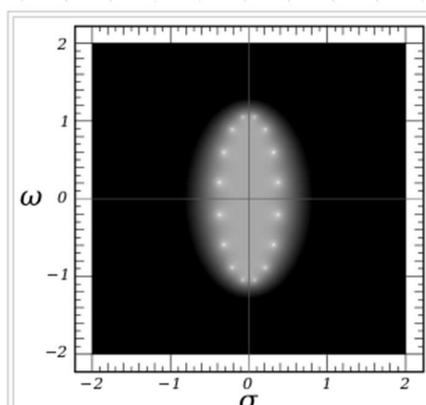


Log of the absolute value of the gain of an 8th order Chebyshev type I filter in complex frequency space ( $s = \sigma + j\omega$ ) with  $\varepsilon = 0.1$  and  $\omega_0 = 1$ . The white spots are poles and are arranged on an ellipse with a semi-axis of 0.3836... in  $\sigma$  and 1.071... in  $\omega$ . The transfer function poles are those poles in the left half plane. Black corresponds to a gain of 0.05 or less, white corresponds to a gain of 20 or more.

## Elliptic Function Response

The response that is **equal-ripple** in both the **passband** and **stopband** is the elliptic function response, as illustrated in Figure 3.5. The transfer function for this type of response is

$$|S_{21}(j\Omega)|^2 = \frac{1}{1 + \varepsilon^2 F_n^2(\Omega)}$$
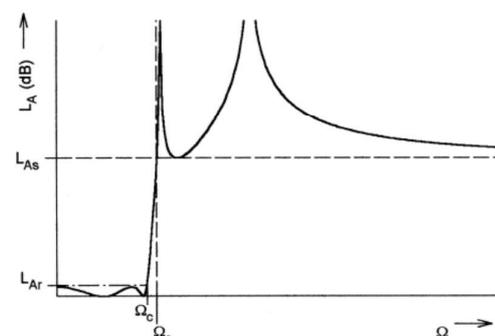
$$F_n(\Omega) = \begin{cases} M \frac{\prod_{i=1}^{n/2} (\Omega_i^2 - \Omega^2)}{\prod_{i=1}^{n/2} (\Omega_s^2/\Omega_i^2 - \Omega^2)} & \text{for } n \text{ even} \\ N \frac{\Omega \prod_{i=1}^{(n-1)/2} (\Omega_i^2 - \Omega^2)}{\prod_{i=1}^{(n-1)/2} (\Omega_s^2/\Omega_i^2 - \Omega^2)} & \text{for } n(\geq 3) \text{ odd} \end{cases}$$


where  $\Omega_i$  ( $0 < \Omega_i < 1$ ) and  $\Omega_s > 1$  represent some critical frequencies;  $M$  and  $N$  are constants to be defined

$F_n(\Omega)$  will oscillate between  $\pm 1$  for  $|\Omega| \leq 1$ , and  $|F_n(\Omega = \pm 1)| = 1$ .

Prof. T. L. Wu

## Elliptic Function Response

Figure 3.6 plots the two typical oscillating curves for  $n = 4$  and  $n = 5$ . Inspection of  $F_n(\Omega)$  in (3.13b) shows that its zeros and poles are inversely proportional, the constant of proportionality being  $\Omega_s$ . An important property of this is that **if  $\Omega_i$  can be found such that  $F_n(\Omega)$  has equal ripples in the passband, it will automatically have equal ripples in the stopband. The parameter  $\Omega_s$  is the frequency at which the equal-ripple stopband starts. For  $n$  even  $F_n(\Omega_s) = M$  is required, which can be used to define the minimum in the stopband for a specified passband ripple constant  $\varepsilon$ .**

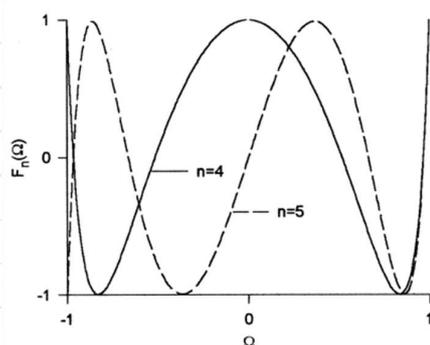


FIGURE 3.6 Plot of elliptic rational function.

Prof. T. L. Wu

## Elliptic Filter

An elliptic filter (also known as a Cauer filter, named after [Wilhelm Cauer](#)) is a [signal processing filter](#) with equalized [ripple \(equiripple\)](#) behavior in both the [passband](#) and the [stopband](#).

The amount of ripple in each band is independently adjustable, and no other filter of equal order can have a faster transition in [gain](#) between the [passband](#) and the [stopband](#), for the given values of ripple (whether the ripple is equalized or not).

As the ripple in the stopband approaches zero, the filter becomes a type I [Chebyshev filter](#).

As the ripple in the passband approaches zero, the filter becomes a type II [Chebyshev filter](#) and finally, as both ripple values approach zero, the filter becomes a [Butterworth filter](#).

Prof. T. L. Wu

## Elliptic Filter

The gain of a [lowpass](#) elliptic filter as a function of angular frequency  $\omega$  is given by:

$$G_n(\omega) = \frac{1}{\sqrt{1 + \epsilon^2 R_n^2(\xi, \omega/\omega_0)}}$$

where  $R_n$  is the  $n$ th-order [elliptic rational function](#) and

$\omega_0$  is the cutoff frequency

$\epsilon$  is the ripple factor


$\xi$  is the selectivity factor

The passband of the gain therefore will vary between 1 and  $1/\sqrt{1 + \epsilon^2}$ .

The gain of the stopband therefore will vary between 0 and  $1/\sqrt{1 + \epsilon^2 L_n^2}$ .

where  $L_n = R_n(\xi, \xi)$

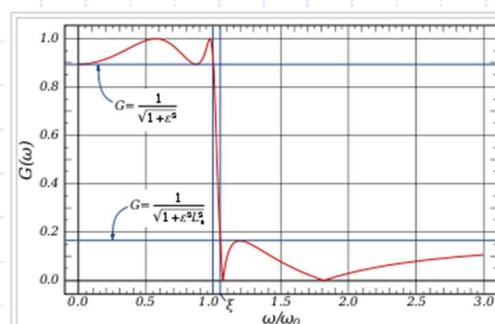
The value of the ripple factor specifies the passband ripple, while the combination of the ripple factor and the selectivity factor specify the stopband ripple.



The frequency response of a fourth-order elliptic low-pass filter with  $\epsilon=0.5$  and  $\xi=1.05$ . Also shown are the minimum gain in the passband and the maximum gain in the stopband, and the transition region between normalized frequency 1 and  $\xi$

Prof. T. L. Wu

# Elliptic Filter

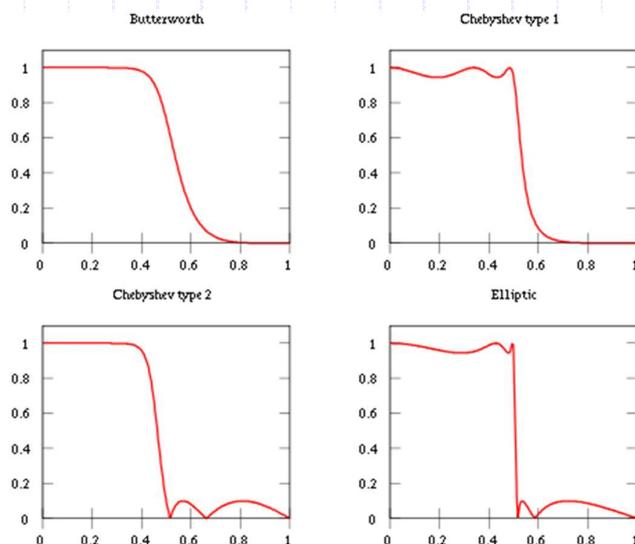


Elliptic filters are sharper than all the others, but they show ripples on the whole bandwidth

Prof. T. L. Wu

# Gaussian (Maximally Flat Group-Delay) Response

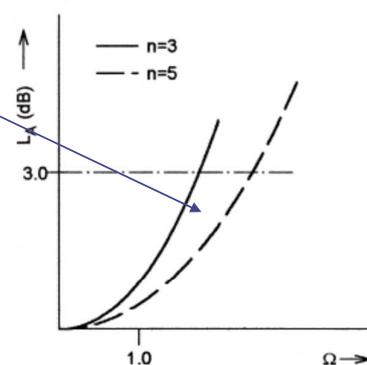1. Poor selectivity
2. BW depends on order  $n$  ?



The Gaussian response is approximated by a rational transfer function

$$S_{21}(p) = \frac{a_0}{\sum_{k=0}^n a_k p^k}$$

where  $p = \sigma + j\Omega$  is the normalized complex frequency variable, and the coefficients

$$a_k = \frac{(2n - k)!}{2^{n-k} k! (n - k)!} \quad (3.15)$$

This transfer function possesses a group delay that has **maximum possible number of zero derivatives with respect to  $\Omega$  at  $\Omega = 0$** , which is why it is said to have maximally flat group delay around  $\Omega = 0$  and is in a sense complementary to the Butterworth response, which has a maximally flat amplitude.

Prof. T. L. Wu

## Gaussian (Maximally Flat Group-Delay) Response

With increasing filter order  $n$ , the selectivity improves little and the insertion loss in decibels approaches the Gaussian form


$$L_A(\Omega) = 10 \log e^{\frac{\Omega^2}{(2n-1)}} \text{ dB}$$

Use of this equation gives the 3 dB bandwidth as

$$\Omega_{3 \text{ dB}} \approx \sqrt{(2n-1) \ln 2}$$

Unlike the Butterworth response, the 3 dB bandwidth of a Gaussian filter is a function of the filter order; the higher the filter order, the wider the 3 dB bandwidth.

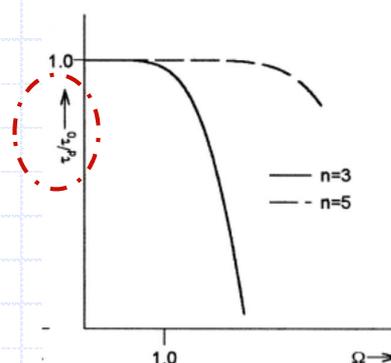Advantage: A quite flat group delay in the passband



F. L. Wu

## All-pass Response

The transfer function of an all-pass network is defined by

$$S_{21}(p) = \frac{D(-p)}{D(p)}$$

where  $p = \sigma + j\Omega$  is the complex frequency variable and  $D(p)$  is a strict Hurwitz polynomial. At real frequencies ( $p = j\Omega$ ),  $|S_{21}(j\Omega)|^2 = S_{21}(p)S_{21}(-p) = 1$  so that the amplitude response is unity at all frequencies, which is why it is called the all-pass network.

However, there will be phase shift and group delay produced by the allpass network.

$$S_{21}(j\Omega) = e^{j\phi_{21}(\Omega)} \longrightarrow \phi_{21}(\Omega) = -j \ln S_{21}(j\Omega)$$

$$\tau_d(\Omega) = -\frac{d\phi_{21}(\Omega)}{d\Omega} = j \frac{d(\ln S_{21}(j\Omega))}{d\Omega}$$

$$\longrightarrow = j \left( \frac{1}{D(-p)} \frac{dD(-p)}{dp} - \frac{1}{D(p)} \frac{dD(p)}{dp} \right) \frac{dp}{d\Omega} \Big|_{p=j\Omega}$$

In [mathematics](#), a Hurwitz polynomial, named after [Adolf Hurwitz](#), is a [polynomial](#) whose coefficients are positive [real numbers](#) and whose zeros are located in the left half-plane of the [complex plane](#), that is, the real part of every zero is negative.

Prof. T. L. Wu

## All-pass Response


An expression for a strict Hurwitz polynomial  $D(p)$  is

$$D(p) = \left( \prod_{k=1}^n [p - (-\sigma_k)] \right) \left( \prod_{k=1}^m [p - (-\sigma_i + j\Omega_i)] [p - (-\sigma_i - j\Omega_i)] \right)$$

If all poles and zeros of an all pass network are located along the  $\sigma$ -axis, such a network is said to consist of C-type sections and therefore referred to as C-type all-pass network.

If the poles and zeros of the transfer function are all complex with quadrantal symmetry about the origin of the complex plane, the resultant network is referred to as D-type all-pass network consisting of D-type sections only.

### C-type (single section)

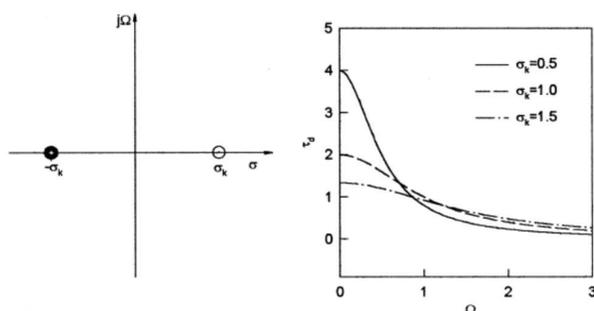

$$S_{21}(p) = \frac{-p + \sigma_k}{p + \sigma_k}$$

$$\tau_d(\Omega) = \frac{2\sigma_k}{\sigma_k^2 + \Omega^2}$$

Prof. T. L. Wu

## All-pass Response

### D-type (single section)

$$S_{21}(p) = \frac{[-p - (-\sigma_i + j\Omega_i)] [-p - (-\sigma_i - j\Omega_i)]}{[p - (-\sigma_i + j\Omega_i)] [p - (-\sigma_i - j\Omega_i)]}$$

$$\tau_d(\Omega) = \frac{4\sigma_i[(\sigma_i^2 + \Omega_i^2) + \Omega^2]}{[(\sigma_i^2 + \Omega_i^2) - \Omega^2]^2 + (2\sigma_i\Omega)^2}$$

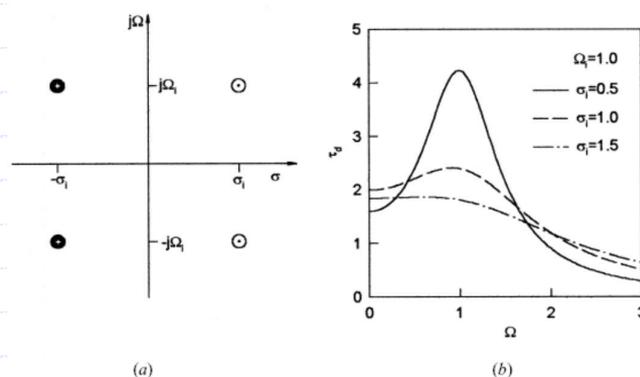


FIGURE 3.9 Characteristics of single-section, D-type, all-pass network: (a) pole-zero diagram, (b) group delay response.

Prof. T. L. Wu

# Lowpass Prototype Filters


Filter syntheses for realizing the transfer functions usually result in the so-called lowpass prototype filters

lowpass prototype filter is in general defined as the lowpass filter whose element values are **normalized to make** the source resistance or conductance equal to **one**, denoted by  $g_0 = 1$ , and the cutoff angular frequency to be unity, denoted by  $\Omega_c = 1$  (rad/s).

$n$ -pole lowpass prototype for realizing an all-pole filter response, including Butterworth, Chebyshev, and Gaussian responses.


## Ladder Network

source resistance

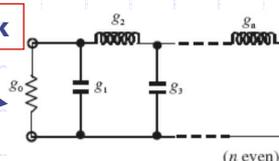

(n even)

load conductance

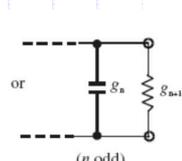


(n odd)

load resistance


## Dual

source conductance

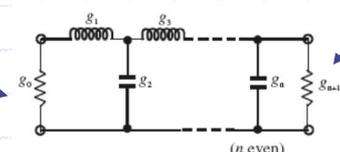

(n even)

load resistance

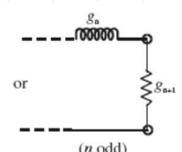

(n odd)

load conductance

These  $g$ -values are supposed to be the inductance in henries, capacitance in farads, resistance in ohms, and conductance in mhos. Prof. T. L. Wu

# Butterworth Lowpass Prototype Filters

$$g_0 = 1.0$$

$$g_i = 2 \sin\left(\frac{(2i-1)\pi}{2n}\right) \quad \text{for } i = 1 \text{ to } n$$

$$g_{n+1} = 1.0$$

To determine the degree of a Butterworth lowpass prototype, a specification that is usually the **minimum stopband attenuation  $L_{As}$  dB at  $\Omega = \Omega_s$  for  $\Omega_s > 1$**  is given.

$$n \geq \frac{\log(10^{0.1L_{As}} - 1)}{2 \log \Omega_s}$$

For example, if  $L_{As} = 40$  dB and  $\Omega_s = 2$ ,  $n \geq 6.644$ , i.e., a 7-pole ( $n = 7$ ) Butterworth prototype should be chosen.

TABLE 3.1 Element values for Butterworth lowpass prototype filters ( $g_0 = 1.0$ ,  $\Omega_c = 1$ ,  $L_{As} = 3.01$  dB at  $\Omega_c$ )

$n$	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$
1	2.0000	1.0								
2	1.4142	1.4142	1.0							
3	1.0000	2.0000	1.0000	1.0						
4	0.7654	1.8478	1.8478	0.7654	1.0					
5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0				
6	0.5176	1.4142	1.9318	1.9318	1.4142	0.5176	1.0			
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0		
8	0.3902	1.1111	1.6629	1.9616	1.9616	1.6629	1.1111	0.3902	1.0	
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	1.0

# Chebyshev Lowpass Prototype Filters

For Chebyshev lowpass prototype filters with a passband ripple  $L_{Ar}$  dB and the cutoff frequency  $\Omega_c = 1$ ,

$$g_0 = 1.0$$

$$g_1 = \frac{2}{\gamma} \sin\left(\frac{\pi}{2n}\right)$$

$$g_i = \frac{1}{g_{i-1}} \frac{4 \sin\left[\frac{(2i-1)\pi}{2n}\right] \sin\left[\frac{(2i-3)\pi}{2n}\right]}{\gamma^2 + \sin^2\left[\frac{(i-1)\pi}{n}\right]} \quad \text{for } i = 2, 3, \dots, n$$

$$g_{n+1} = \begin{cases} 1.0 & \text{for } n \text{ odd} \\ \coth^2\left(\frac{\beta}{4}\right) & \text{for } n \text{ even} \end{cases}$$

$$\beta = \ln\left[\coth^2\left(\frac{L_{Ar}}{17.37}\right)\right]$$

$$\gamma = \sinh\left(\frac{\beta}{2n}\right)$$

For passband ripple  $L_{Ar} = 0.1$  dB

$n$	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$
1	0.3052	1.0								
2	0.8431	0.6220	1.3554							
3	1.0316	1.1474	1.0316	1.0						
4	1.1088	1.3062	1.7704	0.8181	1.3554					
5	1.1468	1.3712	1.9750	1.3712	1.1468	1.0				
6	1.1681	1.4040	2.0562	1.5171	1.9029	0.8618	1.3554			
7	1.1812	1.4228	2.0967	1.5734	2.0967	1.4228	1.1812	1.0		
8	1.1898	1.4346	2.1199	1.6010	2.1700	1.5641	1.9445	0.8778	1.3554	
9	1.1957	1.4426	2.1346	1.6167	2.2054	1.6167	2.1346	1.4426	1.1957	1.0

From [1], p. 100

# Chebyshev Lowpass Prototype Filters

Using the **same example** as given above for the Butterworth prototype, i.e.,  $L_{As} \geq 40$  dB at  $\Omega_s = 2$ , but a passband ripple  $L_{Ar} = 0.1$  dB for the Chebyshev response, we have  $n \geq 5.45$ , i.e.,  $n = 6$  for the Chebyshev prototype to meet this specification.

For the required passband ripple  $L_{Ar}$  dB, the **minimum stopband attenuation  $L_{As}$**  dB at  $\Omega = \Omega_s$ , the degree of a Chebyshev lowpass prototype, which will meet this specification, can be found by


$$n \geq \frac{\cosh^{-1} \sqrt{\frac{10^{0.1L_{As}} - 1}{10^{0.1L_{Ar}} - 1}}}{\cosh^{-1} \Omega_s}$$

Sometimes, the **minimum return loss  $L_R$**  or the maximum voltage standing wave ratio  $VSWR$  in the passband is specified **instead of the passband ripple  $L_{Ar}$** . If the re-


$$L_{Ar} = -10 \log(1 - 10^{0.1L_R}) \text{ dB}$$
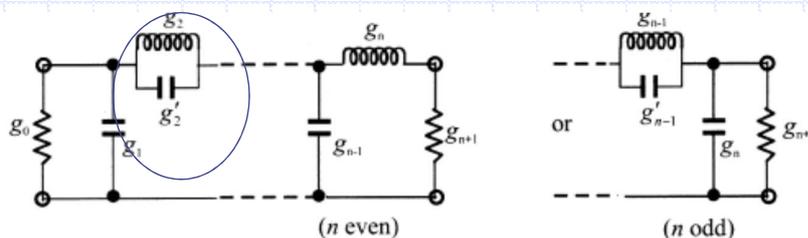
# Elliptic Lowpass Prototype Filters

The series branches of parallel-resonant circuits are introduced for realizing the finite-frequency transmission zeros




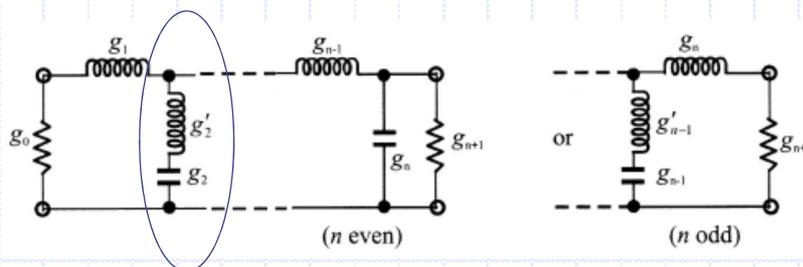
The shunt branches of series-resonant circuits are used for implementing the finite-frequency transmission zeros



Prof. T. L. Wu
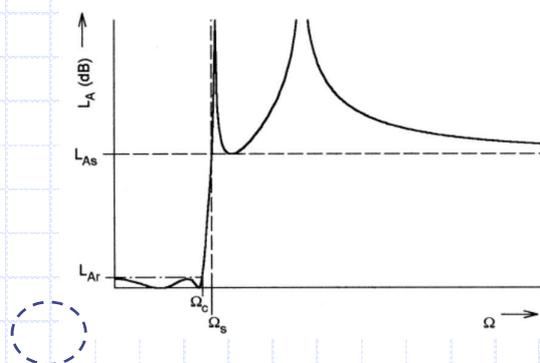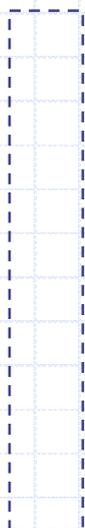
# Elliptic Lowpass Prototype Filters

Unlike the Butterworth and Chebyshev lowpass prototype filters, there is no simple formula available for determining element values of the elliptic function lowpass prototype filters.



instance, considering the same example as used above for the Butterworth and Chebyshev prototype, i.e.,  $L_{As} \geq 40$  dB at  $\Omega_s = 2$  and the passband ripple  $L_{Ar} = 0.1$  dB, we can determine immediately  $n = 5$  by inspecting the design data, i.e.,  $\Omega_s$  and  $L_{As}$  listed in Table 3.3. This also shows that the elliptic function design is superior to both the Butterworth and Chebyshev designs for this type of specification.

## Gaussian Lowpass Prototype Filters

two useful design parameters. The first one is the value of  $\Omega$ , denoted by  $\Omega_{1\%}$ , for which the group delay has fallen off by 1% from its value at  $\Omega = 0$ . Along with this parameter is the insertion loss at  $\Omega_{1\%}$ , denoted by  $L_{\Omega_{1\%}}$  in dB. Not


TABLE 3.4 Element values for Gaussian lowpass prototype filters ( $g_0 = g_{n+1} = 1.0, \Omega_s = 1$ )

$n$	$\Omega_{1\%}$	$L_{\Omega_{1\%}}$ dB	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$
2	0.5627	0.4794	1.5774	0.4226								
3	1.2052	1.3365	1.2550	0.5528	0.1922							
4	1.9314	2.4746	1.0598	0.5116	0.3181	0.1104						
5	2.7090	3.8156	0.9303	0.4577	0.3312	0.2090	0.0718					
6	3.5245	5.3197	0.8377	0.4116	0.3158	0.2364	0.1480	0.0505				
7	4.3575	6.9168	0.7677	0.3744	0.2944	0.2378	0.1778	0.1104	0.0375			
8	5.2175	8.6391	0.7125	0.3446	0.2735	0.2297	0.1867	0.1387	0.0855	0.0289		
9	6.0685	10.3490	0.6678	0.3203	0.2547	0.2184	0.1859	0.1506	0.1111	0.0682	0.0230	
10	6.9495	12.188	0.6305	0.3002	0.2384	0.2066	0.1808	0.1539	0.1240	0.0911	0.0557	0.0187

It is noteworthy that the higher order ( $n \geq 5$ ) Gaussian filters extend the flat group delay property into the frequency range where the insertion loss has exceeded 3 dB.

Prof. T. L. Wu

## All-Pass, Lowpass Prototype Filters

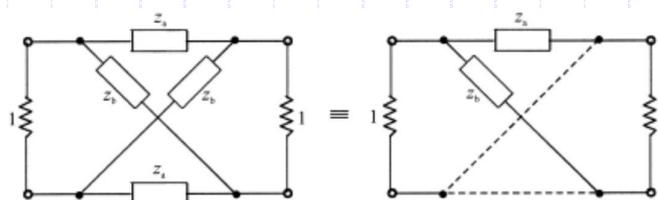

By inspection

$$z_{11} = z_{22} = \frac{z_b + z_d}{2}$$

$$z_{12} = z_{21} = \frac{z_b - z_d}{2}$$




S-parameters can then be derived

Prof. T. L. Wu

# All-Pass, Lowpass Prototype Filters

## C-type

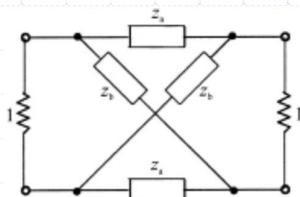

If the elements are assigned as

$$z_a = j\Omega L_a = j\Omega g_1$$

$$z_b = \frac{1}{j\Omega C_a} = \frac{1}{j\Omega g_1}$$

$$g_1 = \frac{1}{\sigma_k}$$

It can be derived that



$$S_{21}(j\Omega) \equiv \frac{z_b - z_a}{z_{11}z_{22} + z_{11} + z_{22} - z_{12}z_{21} + 1}$$

$$= \frac{j\Omega - 1/g_1}{j\Omega + 1/g_1}$$

$$= \frac{p - \sigma_k}{p + \sigma_k}$$



where  $\sigma_k > 0$  is the design parameter that will control the group delay characteristics, as shown in Figure 3.8.

p. 14 in slides

Prof. T. L. Wu

# All-Pass, Lowpass Prototype Filters

## D-type

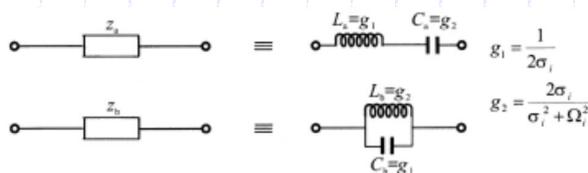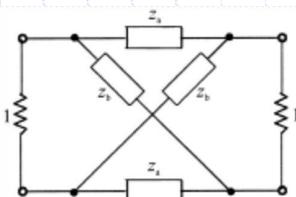

Similar to C-type, the elements are assigned as

$$z_a = j\Omega L_a + \frac{1}{j\Omega C_a}, \quad \frac{1}{z_b} = j\Omega C_b + \frac{1}{j\Omega L_b}$$

$$L_a = C_b = g_1 = \frac{1}{2\sigma_i}, \quad C_a = L_b = g_2 = \frac{2\sigma_i}{\sigma_i^2 + \Omega_i^2}$$

where  $\sigma_i > 0$  and  $\Omega_i > 0$  are the two design parameters that will shape the group delay response, as illustrated in Figure 3.9. Since a D-type section is the second-order all-pass network, there are actually **two lowpass prototype elements**, namely  $g_1$  and  $g_2$ , which will represent both the inductance of an inductor and the capacitance of a capacitor, depending on the locations of these reactive elements, as indicated in Figure 3.12(c).

Prof. T. L. Wu

## FREQUENCY AND ELEMENT TRANSFORMATIONS

- ◆ Frequency and impedance scaling
- ◆ Lowpass Transformation
- ◆ Highpass Transformation
- ◆ Bandpass Transformation
- ◆ Bandpass Transformation

Prof. T. L. Wu

## Impedance and frequency scaling

- ◆ Normalized source resistance/conductance  $\rightarrow g_0 = 1$
- ◆ Cutoff frequency  $\rightarrow \Omega_c = 1$ 
  - impedance scaling : define an impedance scaling factor  $\gamma_0$

$$\gamma_0 = \begin{cases} Z_0/g_0 & \text{for } g_0 \text{ being the resistance} \\ g_0/Y_0 & \text{for } g_0 \text{ being the conductance} \end{cases}$$

Scaled value : impedance  $\rightarrow$  impedance  $\times \gamma_0$

$$L \rightarrow \gamma_0 L \quad C \rightarrow C/\gamma_0$$

$$R \rightarrow \gamma_0 R \quad G \rightarrow G/\gamma_0$$

The impedance scaling will remove the  $g_0 = 1$  normalization and adjust the filter to work for any value of the source impedance denoted by  $Z_0$ . This scaling will have no effect on the response shape.

Resistive element transformation for the generic term  $g$  for the lowpass prototype elements in the element transformation

$$R = \gamma_0 g \quad \text{for } g \text{ representing the resistance}$$

$$G = \frac{g}{\gamma_0} \quad \text{for } g \text{ representing the conductance}$$

Prof. T. L. Wu

## Impedance and frequency scaling

♥ Frequency scaling :  $\Omega = \left(\frac{\Omega_c}{\omega_c}\right)\omega \Rightarrow |S'_{21}(j\Omega)|^2 = \left|S_{21}\left(j\frac{\Omega_c}{\omega_c}\omega\right)\right|^2$

scaled values :

$$j\Omega L = j\left(\frac{\Omega_c}{\omega_c}\right)\omega L \Rightarrow L' = \left(\frac{\Omega_c}{\omega_c}\right)L \quad \frac{1}{j\Omega C} = \frac{1}{j\left(\frac{\Omega_c}{\omega_c}\right)\omega C} \Rightarrow C' = \left(\frac{\Omega_c}{\omega_c}\right)C$$

♥ Impedance and Frequency scaling :

scaled values :


$$L = \left(\frac{\Omega_c}{\omega_c}\right)\gamma_0 g \quad \text{for } g \text{ representing the inductance}$$

$$C = \left(\frac{\Omega_c}{\omega_c}\right)\frac{g}{\gamma_0} \quad \text{for } g \text{ representing the capacitance}$$

Prof. T. L. Wu
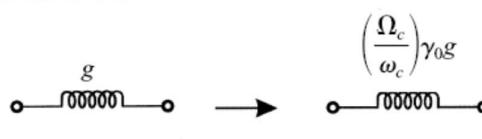
## Lowpass Transformation

$$L = \left(\frac{\Omega_c}{\omega_c}\right)\gamma_0 g \quad \text{for } g \text{ representing the inductance}$$




$$C = \left(\frac{\Omega_c}{\omega_c}\right)\frac{g}{\gamma_0} \quad \text{for } g \text{ representing the capacitance}$$


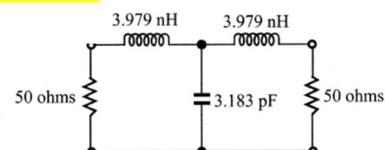
### Example:

To demonstrate the use of the element transformation, let us consider design of a practical lowpass filter with a cutoff frequency  $f_c = 2 \text{ GHz}$  and a source impedance  $Z_0 = 50 \text{ ohms}$ . A 3-pole Butterworth lowpass prototype with the structure of Figure 3.10(b) is chosen for this example, which gives  $g_0 = g_4 = 1.0 \text{ mhos}$ ,  $g_1 = g_3 = 1.0 \text{ H}$ , and  $g_2 = 2.0 \text{ F}$  for  $\Omega_c = 1.0 \text{ rad/s}$ , from Table 3.1. The impedance scaling factor is  $\gamma_0 = 50$ , according to (3.34). The angular cutoff frequency  $\omega_c = 2\pi \times 2 \times 10^9 \text{ rad/s}$ . Applying (3.38), we find  $L_1 = L_3 = 3.979 \text{ nH}$  and  $C_2 = 3.183 \text{ pF}$ . The resultant lowpass filter is illustrated in Figure 3.13(b).



# Highpass Transformation



$$\because 0 \rightarrow \pm\infty, \Omega_c \rightarrow -\omega_c, -\Omega_c \rightarrow \omega_c \Rightarrow \Omega = -\frac{\omega_c \Omega_c}{\omega}$$

$$\frac{1}{j\Omega \frac{C}{\gamma_0}} = \frac{1}{j\left(-\frac{\omega_c \Omega_c}{\omega}\right) \frac{C}{\gamma_0}} = j\omega L' \Rightarrow L' = \left(\frac{1}{\omega_c \Omega_c}\right) \frac{\gamma_0}{C}$$

$$j\Omega \gamma_0 L = j\left(-\frac{\omega_c \Omega_c}{\omega}\right) \gamma_0 L = \frac{1}{j\omega C'} \Rightarrow C' = \left(\frac{1}{\omega_c \Omega_c}\right) \frac{1}{\gamma_0 L}$$

Prof. T. L. Wu


# Highpass Transformation

An inductive/capacitive element in the lowpass prototype will be inversely transformed to a capacitive/inductive element in the highpass filter.

$$\Omega = -\frac{\omega_c \Omega_c}{\omega} \longrightarrow j\Omega g \rightarrow \frac{\omega_c \Omega_c g}{j\omega}$$



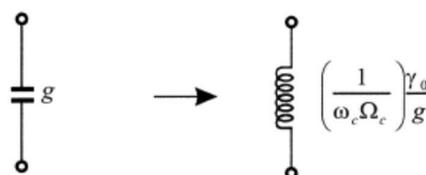
$$C = \left(\frac{1}{\omega_c \Omega_c}\right) \frac{1}{\gamma_0 g} \quad \text{for } g \text{ representing the inductance}$$




$$L = \left(\frac{1}{\omega_c \Omega_c}\right) \frac{\gamma_0}{g} \quad \text{for } g \text{ representing the capacitance}$$

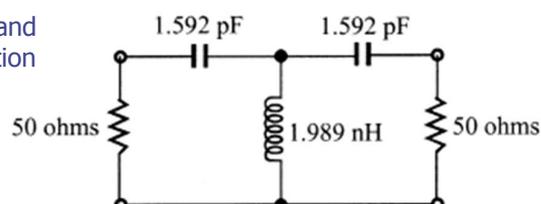Example:

A practical highpass filter with a cutoff frequency at 2GHz and 50-ohms terminals, which is obtained from the transformation of the 3 pole Butterworth lowpass prototype given above.



# Bandpass Transformation

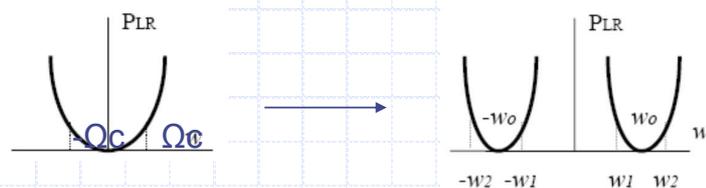

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

$$FBW = \frac{\omega_2 - \omega_1}{\omega_0}$$

$$0 \rightarrow \omega_0, \Omega_c \rightarrow \omega_2, -\Omega_c \rightarrow \omega_1, \Omega = \frac{\Omega_c}{FBW} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)$$


$$\frac{1}{j\Omega \frac{C}{\gamma_0}} = \frac{1}{j \frac{\Omega_c}{FBW} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \frac{C}{\gamma_0}} = \frac{1}{j\omega \left( \frac{\Omega_c}{FBW \omega_0} \right) \frac{C}{\gamma_0} + \frac{1}{j\omega \left( \frac{FBW}{\omega_0 \Omega_c} \right) \frac{\gamma_0}{C}}} \Rightarrow C_p = \left( \frac{\Omega_c}{FBW \omega_0} \right) \frac{C}{\gamma_0}, L_p = \left( \frac{FBW}{\omega_0 \Omega_c} \right) \frac{\gamma_0}{C}$$

$$j\Omega \gamma_0 L = j \frac{\Omega_c}{FBW} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \gamma_0 L = j\omega \left( \frac{\Omega_c}{FBW \omega_0} \right) \gamma_0 L + \frac{1}{j\omega \left( \frac{FBW}{\omega_0 \Omega_c} \right) \frac{1}{\gamma_0 L}} \Rightarrow C_s = \left( \frac{FBW}{\omega_0 \Omega_c} \right) \frac{1}{\gamma_0 L}, L_s = \left( \frac{\Omega_c}{FBW \omega_0} \right) \gamma_0 L$$

Prof. T. L. Wu

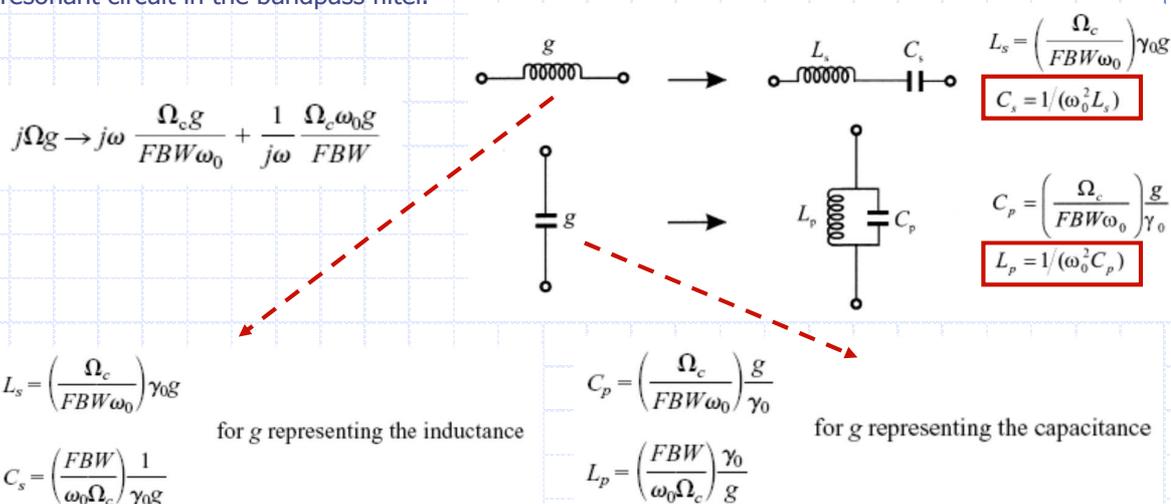
# Bandpass Transformation

An inductive/capacitive element  $g$  in the lowpass prototype will transform to a series/parallel LC resonant circuit in the bandpass filter.



Prof. T. L. Wu

# Bandstop Transformation

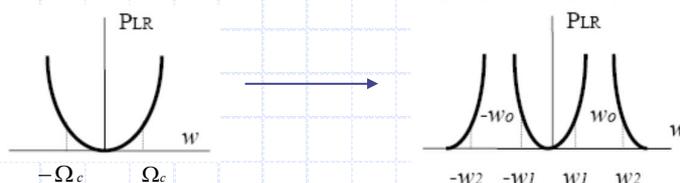

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

$$FBW = \frac{\omega_2 - \omega_1}{\omega_0}$$

$$0 \rightarrow \pm\infty, \Omega_c \rightarrow \omega_1, -\Omega_c \rightarrow \omega_2 \Rightarrow \Omega = \frac{\Omega_c FBW}{\left(\frac{\omega_0}{\omega} - \frac{\omega}{\omega_0}\right)}$$

$$j\Omega\gamma_0 L = j \frac{\Omega_c FBW}{\left(\frac{\omega_0}{\omega} - \frac{\omega}{\omega_0}\right)} \gamma_0 L = \frac{1}{\frac{\omega_0}{j\omega\Omega_c FBW \gamma_0 L} + j\omega \frac{1}{FBW \omega_0 \Omega_c \gamma_0 L}} \Rightarrow C_p = \left(\frac{1}{FBW \omega_0 \Omega_c}\right) \frac{1}{\gamma_0 L}, L_p = \left(\frac{\Omega_c FBW}{\omega_0}\right) \gamma_0 L$$

$$\frac{1}{j\Omega \frac{C}{\gamma_0}} = \frac{1}{j \frac{\Omega_c FBW}{\left(\frac{\omega_0}{\omega} - \frac{\omega}{\omega_0}\right)} \frac{C}{\gamma_0}} = \frac{1}{j\omega \left(\frac{\Omega_c FBW}{\omega_0}\right) \frac{C}{\gamma_0}} + j\omega \frac{1}{FBW \omega_0 \Omega_c} \frac{\gamma_0}{C} \Rightarrow C_s = \left(\frac{\Omega_c FBW}{\omega_0}\right) \frac{C}{\gamma_0}, L_s = \frac{1}{FBW \omega_0 \Omega_c} \frac{\gamma_0}{C}$$

Prof. T. L. Wu

# Bandstop Transformation

Opposite to the bandpass transformation, an inductive/capacitive element  $g$  in the lowpass prototype will transform to a parallel/series  $LC$  resonant circuit in the bandstop filter.

$$\Omega = \frac{\Omega_c FBW}{\left(\frac{\omega_0}{\omega} - \frac{\omega}{\omega_0}\right)}$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

$$FBW = \frac{\omega_2 - \omega_1}{\omega_0}$$

$$C_p = \left(\frac{1}{FBW \omega_0 \Omega_c}\right) \frac{1}{\gamma_0 g}$$


for  $g$  representing the inductance

$$L_p = \left(\frac{\Omega_c FBW}{\omega_0}\right) \gamma_0 g$$


$$L_s = \left(\frac{1}{FBW \omega_0 \Omega_c}\right) \frac{\gamma_0}{g}$$

for  $g$  representing the capacitance
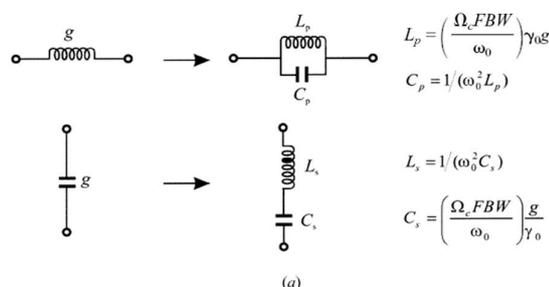
$$C_s = \left(\frac{\Omega_c FBW}{\omega_0}\right) \frac{g}{\gamma_0}$$



Ex:

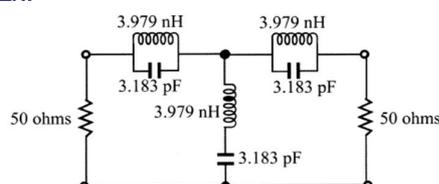

Prof. T. L. Wu

# IMMITTANCE INVERTERS

- ◆ Definition of Immittance, Impedance, and Admittance Inverters
- ◆ Filters with Immittance Inverters
- ◆ Practical Realization of Immittance Inverters

Prof. T. L. Wu

## Definition of Immittance

- ◆ Immittance inverters are either impedance or admittance inverters.
- ◆ An idealized impedance inverter is a two-port network that has a unique property at all frequencies
- ◆ if it is terminated in an impedance  $Z_2$  on one port, the impedance  $Z_1$  seen looking in at the other port is

$$Z_1 = \frac{K^2}{Z_2}$$

$K$ : characteristic impedance of the inverter

- ◆ As can be seen, if  $Z_2$  is inductive/conductive,  $Z_1$  will become conductive/inductive, and hence the inverter has a phase shift of  $\pm 90$  degrees or an odd multiple thereof.

Prof. T. L. Wu


## Impedance/admittance Inverter

- ◆ the inverter has a phase shift of  $\pm 90$  degrees
- ◆ Impedance/admittance inverters are also known as  $K$ -inverters /  $J$ -inverters.
- ◆ The  $ABCD$  matrix of ideal impedance inverters may generally be expressed as


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0 & \mp jK \\ \pm \frac{1}{jK} & 0 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0 & \pm \frac{1}{jJ} \\ \mp jJ & 0 \end{bmatrix}$$

Impedance inverter  
or  $K$ -inverter

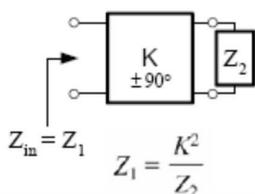

admittance inverter  
or  $J$ -inverter

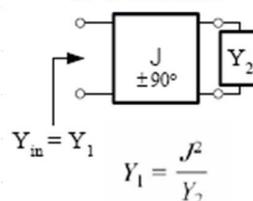


It is noted that the  $\pm 90$  degree is decided by the phase of  $S_{21}$  of the 2-port network

Prof. T. L. Wu
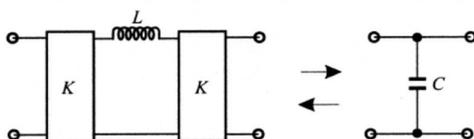
## Filters with Immittance Inverters


A series inductance with an inverter on each side looks like a shunt capacitance from its exterior terminals



Proved by ABCD matrix

$$\begin{bmatrix} 0 & jK \\ -\frac{1}{jK} & 0 \end{bmatrix} \begin{bmatrix} 1 & j\omega L \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & jK \\ -\frac{1}{jK} & 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ j\omega C & 1 \end{bmatrix}$$

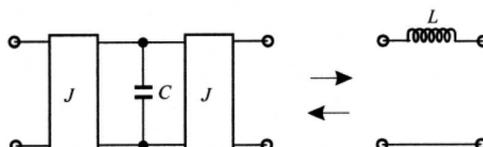A shunt capacitance with an inverter on each side looks like a series inductance from its external terminals




Inverters have the ability to shift impedance or admittance levels depending on the choice of  $K$  or  $J$  parameters.

Making use of these properties enables us to convert a filter circuit to an equivalent form that would be more convenient for implementation with microwave structures.

Prof. T. L. Wu

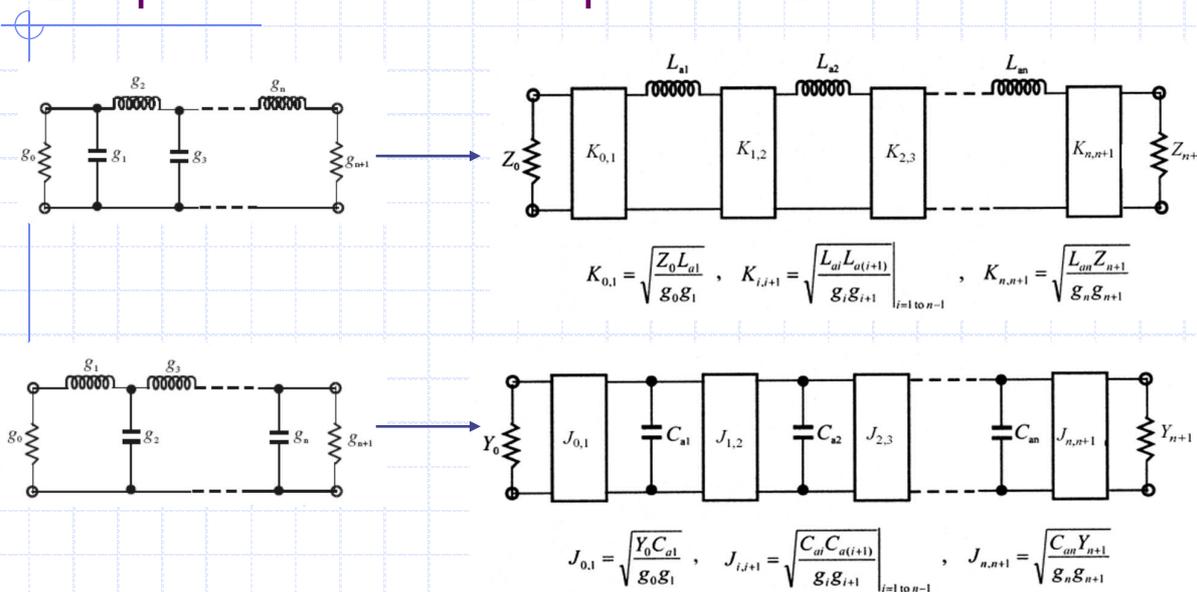
# Lowpass Filters with Impedance Inverters



The new element values, such as  $Z_0$ ,  $Z_{n+1}$ ,  $L_{ai}$ ,  $Y_0$ ,  $Y_{n+1}$ , and  $C_{ai}$ , may be chosen arbitrarily and the filter response will be identical to that of the original prototype, provided that the immittance inverter parameters  $K_{i,j+1}$  and  $J_{i,j+1}$  are specified as indicated by the equations in Figure 3.18.

Prof. T. L. Wu
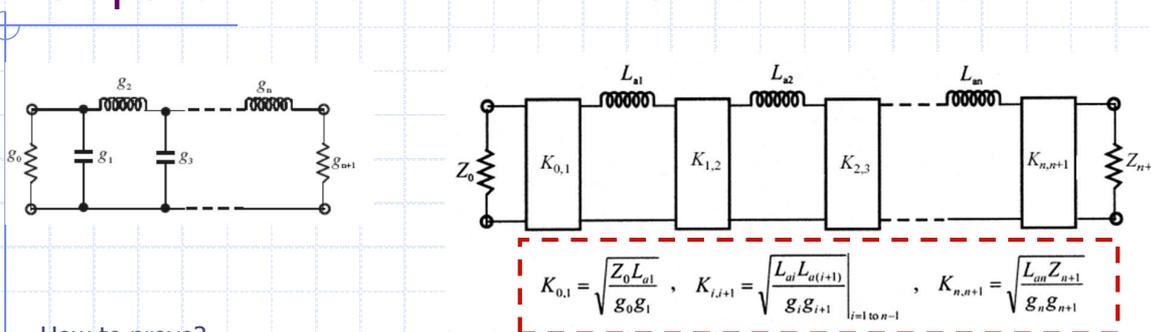
# Lowpass Filters with Admittance Inverters



How to prove?

Take  $n=2$  as an example

By expanding the input immittances of the original prototype networks and the equivalent ones in continued fractions and by equating corresponding terms.

$$Z(s) = \frac{1}{\frac{1}{g_3 + s g_2} + g_1}$$


← Compare their coefficients →

$$\tilde{Z}(s) = \frac{K_{01}^2}{s L_{a2} + \frac{K_{23}^2}{Z_3} + (s L_{a1})}$$

As an example  $\frac{g_1}{(Z_0 / g_0)} = \frac{L_{a1}}{K_{01}^2} \therefore K_{01} = \sqrt{\frac{L_{a1} Z_0}{g_1 g_0}}$

Prof. T. L. Wu
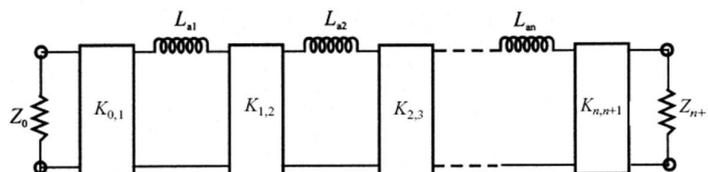
## Bandpass Filters with Impedance Inverters



Since the source impedances are assumed the same in both filters as indicated, no impedance scaling is required.


$$K_{0,1} = \sqrt{\frac{Z_0 L_{a1}}{g_0 g_1}}, \quad K_{i,i+1} = \sqrt{\frac{L_{ai} L_{a(i+1)}}{g_i g_{i+1}}}, \quad K_{n,n+1} = \sqrt{\frac{L_{an} Z_{n+1}}{g_n g_{n+1}}}$$

transforming the inductors of the lowpass filter to the series resonators of the bandpass filter, we obtain:

Replace  $L_{a1}$

$$L_{si} = \left( \frac{\Omega_c}{FBW \omega_0} \right) L_{ai}$$

$$C_{si} = \frac{1}{\omega_0^2 L_{si}}$$

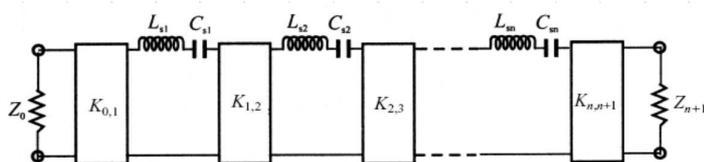


$$K_{0,1} = \sqrt{\frac{Z_0 FBW \omega_0 L_{s1}}{\Omega_c g_0 g_1}}, \quad K_{i,i+1} = \frac{FBW \omega_0}{\Omega_c} \sqrt{\frac{L_{si} L_{s(i+1)}}{g_i g_{i+1}}}, \quad K_{n,n+1} = \sqrt{\frac{FBW \omega_0 L_{sn} Z_{n+1}}{\Omega_c g_n g_{n+1}}}$$

$$C_{si} = \frac{1}{\omega_0^2 L_{si}} \Big|_{i=1 \text{ to } n}$$


Prof. T. L. Wu

## Bandpass Filters with admittance Inverters

Similarly

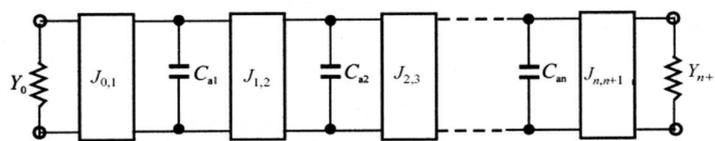
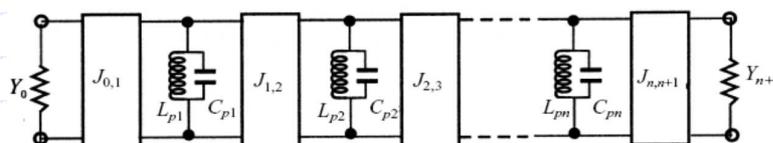
$$J_{0,1} = \sqrt{\frac{Y_0 C_{a1}}{g_0 g_1}}, \quad J_{i,i+1} = \sqrt{\frac{C_{ai} C_{a(i+1)}}{g_i g_{i+1}}}, \quad J_{n,n+1} = \sqrt{\frac{C_{an} Y_{n+1}}{g_n g_{n+1}}}$$



$$J_{0,1} = \sqrt{\frac{Y_0 FBW \omega_0 C_{p1}}{\Omega_c g_0 g_1}}, \quad J_{i,i+1} = \frac{FBW \omega_0}{\Omega_c} \sqrt{\frac{C_{pi} C_{p(i+1)}}{g_i g_{i+1}}}, \quad J_{n,n+1} = \sqrt{\frac{FBW \omega_0 C_{pn} Y_{n+1}}{\Omega_c g_n g_{n+1}}}$$

$$L_{pi} = \frac{1}{\omega_0^2 C_{pi}} \Big|_{i=1 \text{ to } n}$$


Prof. T. L. Wu

# Generalized bandpass filters (including distributed elements) using immittance inverters.

Reactance slope parameter for resonators having zero reactance at center frequency

$$x = \frac{\omega_0}{2} \frac{dX(\omega)}{d\omega} \Big|_{\omega=\omega_0}$$

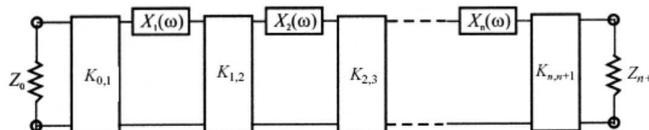a lumped LC series resonator is  $\omega_0 L$ .




$$K_{0,1} = \sqrt{\frac{Z_0 FBW x_1}{\Omega_c g_0 g_1}}, \quad K_{i,j+1} = \frac{FBW}{\Omega_c} \sqrt{\frac{x_i x_{i+1}}{g_i g_{i+1}}}, \quad K_{n,n+1} = \sqrt{\frac{FBW x_n Z_{n+1}}{\Omega_c g_n g_{n+1}}}$$

Susceptance slope parameter for resonators having zero susceptance at center frequency

$$b = \frac{\omega_0}{2} \frac{dB(\omega)}{d\omega} \Big|_{\omega=\omega_0}$$

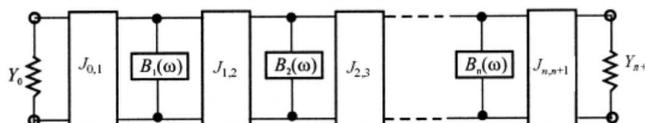a lumped LC parallel resonator is  $\omega_0 C$ .



$$J_{0,1} = \sqrt{\frac{Y_0 FBW b_1}{\Omega_c g_0 g_1}}, \quad J_{i,j+1} = \frac{FBW}{\Omega_c} \sqrt{\frac{b_i b_{i+1}}{g_i g_{i+1}}}, \quad J_{n,n+1} = \sqrt{\frac{FBW b_n Y_{n+1}}{\Omega_c g_n g_{n+1}}}$$


$$x_i = \frac{\omega_0}{2} \frac{dX_i(\omega)}{d\omega} \Big|_{\omega=\omega_0}$$

$$b_i = \frac{\omega_0}{2} \frac{dB_i(\omega)}{d\omega} \Big|_{\omega=\omega_0}$$

Prof. T. L. Wu


## Practical Realization of Immittance Inverters

impedance inverter

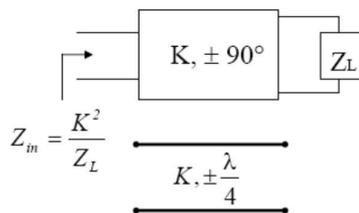


$$Z_{in} = \frac{K^2}{Z_L}$$

proof

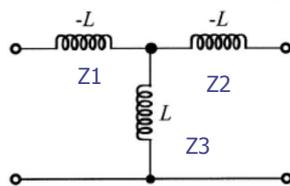


$$K = \omega L \quad +90^\circ$$

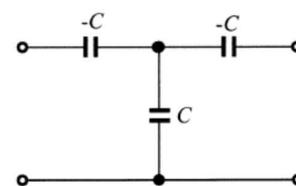


$$K = \frac{1}{\omega C} \quad -90^\circ$$

admittance inverter

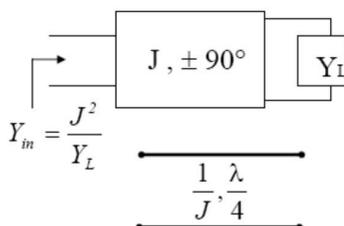


$$Y_{in} = \frac{J^2}{Y_L}$$
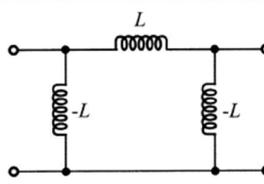
$$\begin{bmatrix} 1 + \frac{Z_1}{Z_3} & Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3} \\ \frac{1}{Z_3} & 1 + \frac{Z_2}{Z_3} \end{bmatrix} = \begin{bmatrix} 0 & -j\omega L \\ \frac{1}{j\omega L} & 0 \end{bmatrix}$$


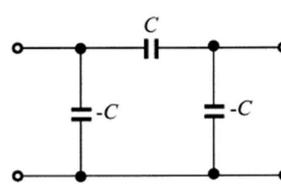
$$J = \frac{1}{\omega L} \quad -90^\circ$$




$$J = \omega C \quad +90^\circ$$

Prof. T. L. Wu
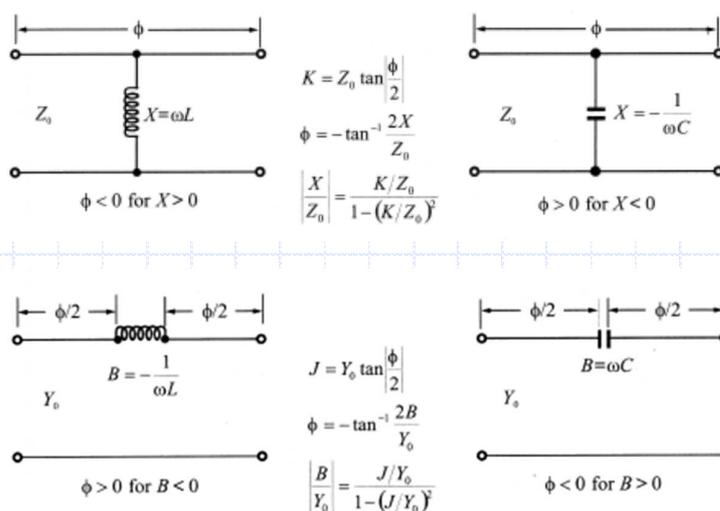
## Immittance inverters comprised of lumped and transmission line elements

- ◆ A circuit mixed with lumped and transmission line elements



Prof. T. L. Wu

## Richards' Transformation

Distributed transmission line elements are of importance for designing practical microwave filters.


A commonly used approach to the design of a practical distributed filter is to seek some approximate equivalence between lumped and distributed elements.

Such equivalence can be established by applying [Richards's transformation](#)

Richards showed that distributed networks, comprised of commensurate length (equal electrical length) transmission lines and lumped resistors, could be treated in analysis or synthesis [as lumped element LCR networks under the transformation](#)


The new complex plane where  $t$  is defined is called the *t-plane*.

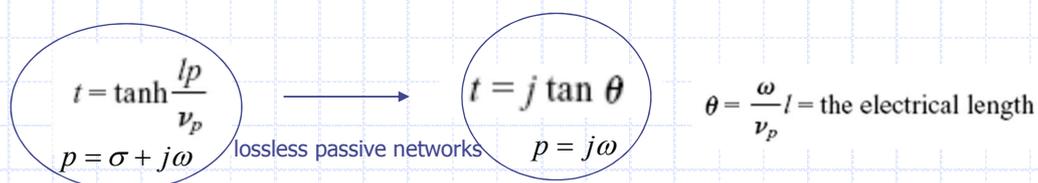Following is referred to as Richards' transformation



Prof. T. L. Wu

# Richards' Transformation

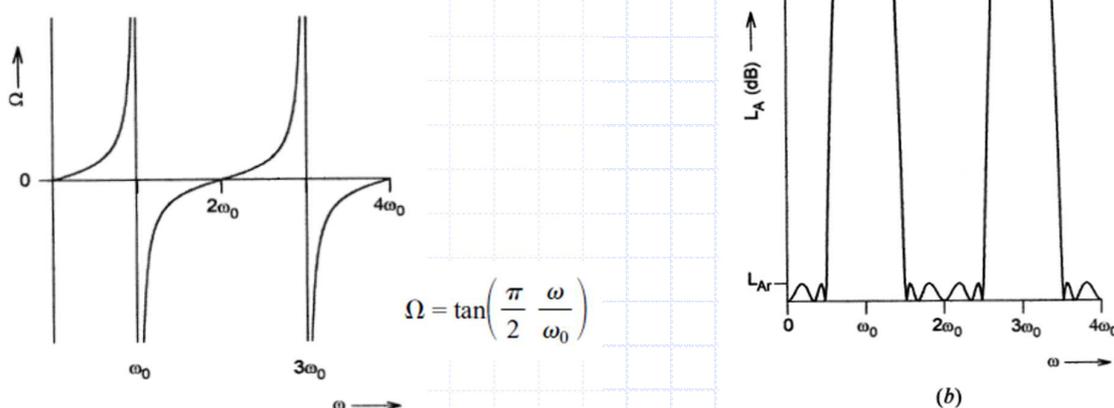


The periodic frequency response of the distributed filter network is demonstrated in Figure 3.23(b), which is obtained by applying the Richards' transformation of (3.54) to the Chebyshev lowpass prototype transfer function of (3.9), showing that the response repeats in frequency intervals of  $2\omega_0$ .

A lowpass response in the *p-plane* may be mapped into either the *lowpass* or the *bandstop* one in the *t-plane*, depending on the design objective. Similarly, it can be shown that a *highpass* response in the *p-plane* may be transformed as either the *highpass* or the *bandpass* one in the *t-plane*.

Prof. T. L. Wu
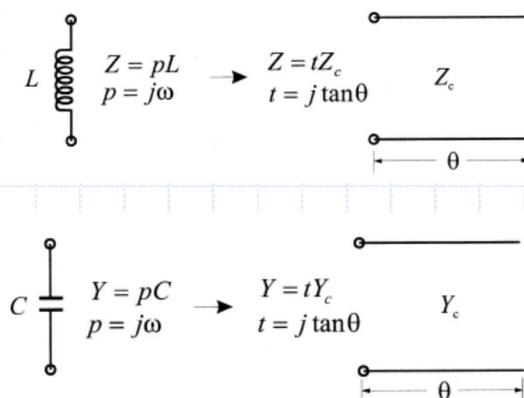
# Richards' Transformation


Lumped and distributed element correspondence under Richards' transformation



Prof. T. L. Wu
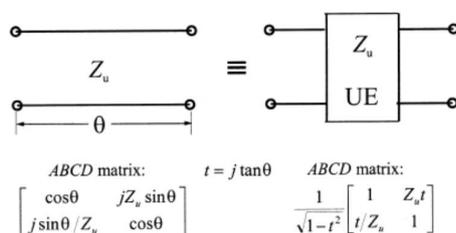
# Richards' Transformation

Another important distributed element, which has no lumped-element counterpart, is a two-port network consisting of a commensurate-length line.




It is interesting to note that the **unit element** has a half-order transmission zero at  $t = \pm 1$ .

Unit elements are usually employed to separate the circuit elements in distributed filters, which are otherwise located at the same physical point.
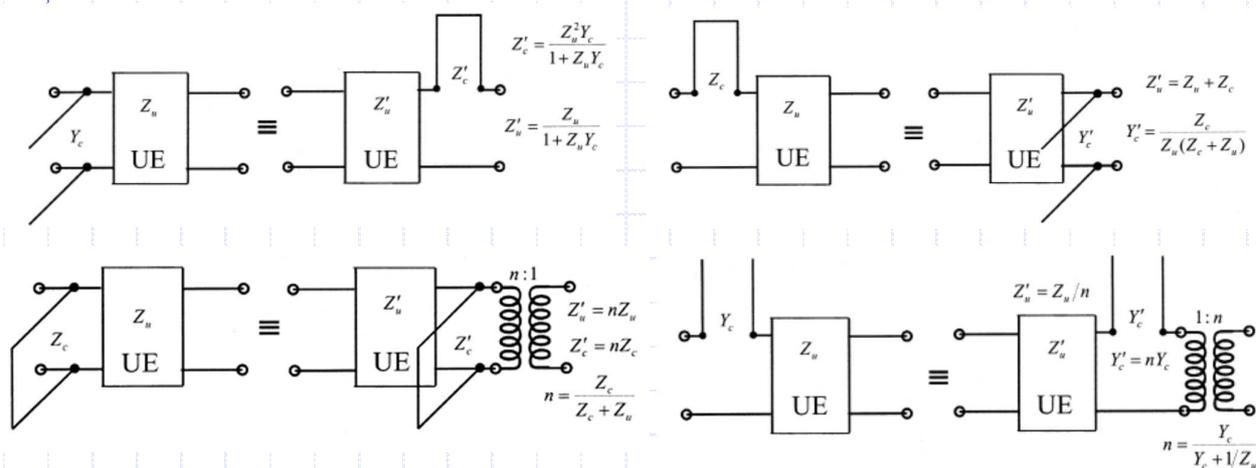
# Kuroda Identities


Such transformations not only provide designers with flexibility, but also are essential in many cases to obtain networks that are physically realizable with physical dimensions.

- Physically separate transmission line stubs
- Transform series stubs into shunt stubs, or vice versa
- Change impractical characteristic impedances into more realizable ones



# Kuroda Identities


Proof:

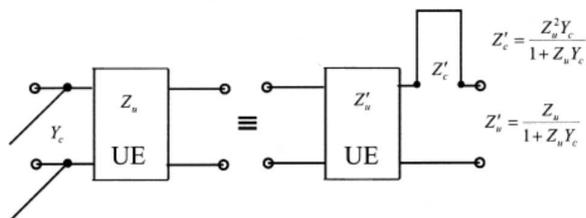

$$\frac{1}{\sqrt{1-t^2}} \begin{bmatrix} 1 & 0 \\ Y_c t & 1 \end{bmatrix} \begin{bmatrix} 1 & Z_u t \\ t/Z_u & 1 \end{bmatrix} = \frac{1}{\sqrt{1-t^2}} \begin{bmatrix} 1 & Z_u t \\ (Y_c + 1/Z_u)t & Y_c Z_u t^2 + 1 \end{bmatrix} \iff \frac{1}{\sqrt{1-t^2}} \begin{bmatrix} 1 & Z'_u t \\ t/Z'_u & 1 \end{bmatrix} \begin{bmatrix} 1 & Z'_c t \\ 0 & 1 \end{bmatrix} = \frac{1}{\sqrt{1-t^2}} \begin{bmatrix} 1 & (Z'_u + Z'_c)t \\ t/Z'_u & Z'_c/Z'_u t^2 + 1 \end{bmatrix}$$

Prof. T. L. Wu


# Kuroda identities

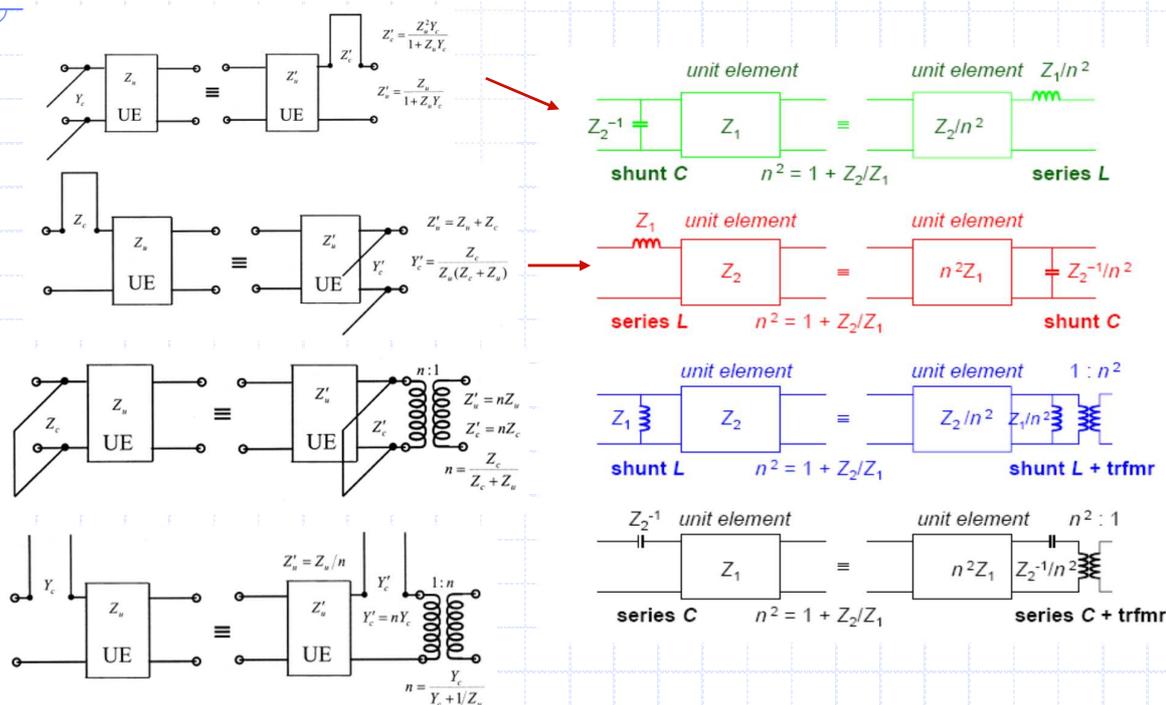


Prof. T. L. Wu

# Coupled-Line Equivalent Circuits

## Coupled line

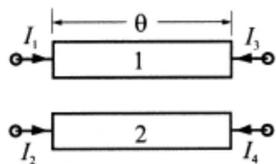

## Single line

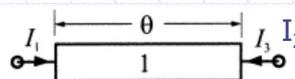

Similar form

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \frac{v_p}{t} \begin{bmatrix} [L] & \sqrt{1-t^2}[L] \\ \sqrt{1-t^2}[L] & [L] \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -jZ_0 \cot \theta & -jZ_0 \csc \theta \\ -jZ_0 \csc \theta & -jZ_0 \cot \theta \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$= \frac{v_p}{t} \begin{bmatrix} L & L/\sqrt{1-t^2} \\ \sqrt{1-t^2}L & L \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[L] = \begin{bmatrix} L_{11} & L_{12} \\ L_{12} & L_{22} \end{bmatrix}$$

Proof: refer to "Microwave Engineering"

In this case  $L_{11}$  and  $L_{22}$  are the self-inductance per unit length of line 1 and line 2, respectively, and  $L_{12}$  is the mutual inductance per unit length. If the coupled lines are symmetrical,  $L_{11} = L_{22}$ . It may be remarked that  $[L]$  and  $[C]$  together satisfy


$$[L] \cdot [C] = [C] \cdot [L] = [U] / v_p^2 \quad (3.58)$$

where  $[U]$  denotes the identity matrix.

Prof. T. L. Wu

# Coupled-Line Equivalent Circuits

## Admittance matrix form

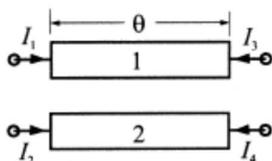


$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \frac{v_p}{t} \begin{bmatrix} [C] & -\sqrt{1-t^2}[C] \\ -\sqrt{1-t^2}[C] & [C] \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}$$

$$[C] = \begin{bmatrix} C_{11} & -C_{12} \\ -C_{12} & C_{22} \end{bmatrix}$$




$C_{11}$  and  $C_{22}$  are the self-capacitance per unit length of line 1 and line 2 respectively, and  $C_{12}$  is the mutual capacitance per unit length. Note that  $C_{11} = C_{22}$  if the coupled lines are symmetrical.

Prof. T. L. Wu

# Coupled-Line Equivalent Circuits

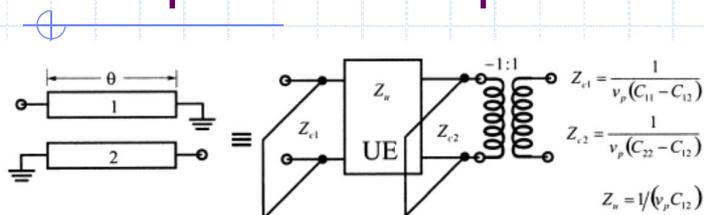

It can be proved by ABCD parameters

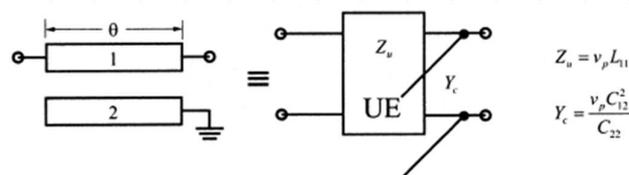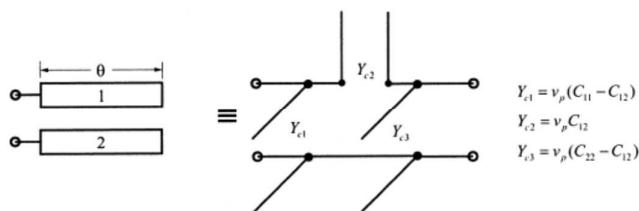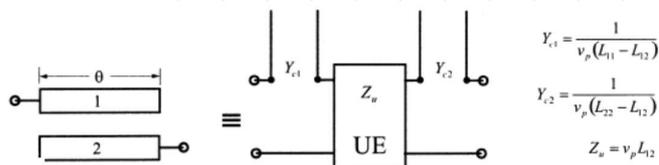



Prof. T. L. Wu

# Dissipation and unloaded quality factor



In reality, any practical microwave filter will have lossy elements with finite unloaded quality factors in association with power dissipation in these elements.

Such parasitic dissipation may frequently lead to substantial differences between the response of the filter actually realized and that of the ideal one designed with lossless elements.

## Unloaded quality factor

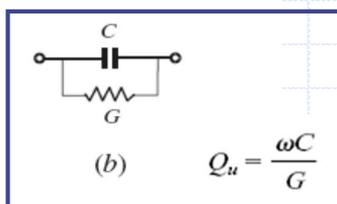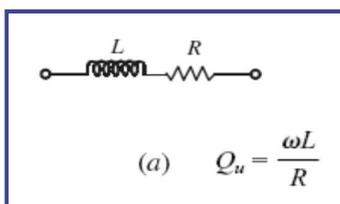

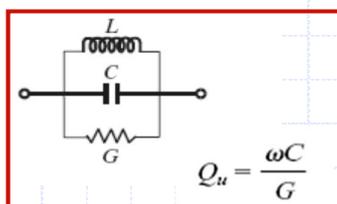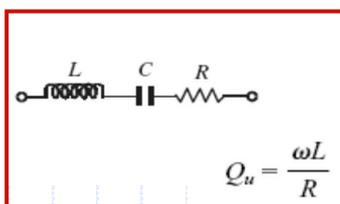For a lowpass or a highpass filter,  $\omega$  is usually the cutoff frequency; while for a bandpass or bandstop filter, is the center frequency.



$\omega$  is the resonant freq. for the lossy resonator

Prof. T. L. Wu

## Dissipation Effect on Lowpass and Highpass Filters

Assuming that the unloaded quality factors of all reactive elements in a filter are known, determined theoretically or experimentally, we can find  $R$  and  $G$  for the lossy reactive elements from previous equations. The dissipation effects on the filter insertion loss response can easily be estimated by analysis of the whole filter equivalent circuit, including the dissipative elements  $R$  and  $G$ .

Another approach based on simple formula by Cohn (1959)

$$\Delta L_{A0} = 4.343 \sum_{i=1}^n \frac{\Omega_c}{Q_{ui}} g_i \text{ dB}$$

where  $\Delta L_{A0}$  is the dB increase in insertion loss at  $\omega = 0$ ,  $\Omega_c$  and  $g_i$  are the **cutoff frequency** and element values of the lowpass prototypes, as discussed previously in this chapter, and  $Q_{ui}$  are the unloaded quality factors of microwave elements corresponding to  $g_i$ , which are given at the **cutoff  $\omega_c$**  of the practical lowpass filters. This



Prof. T. L. Wu

## Dissipation Effect on Lowpass and Highpass Filters

As an example, let us consider the lowpass filter designed previously in Figure 3.13, which has a Butterworth response with a cutoff frequency at  $f_c = 2$  GHz. To take into account the finite unloaded quality factors of the reactive elements, the filter circuit becomes that of Figure below.

Two effects are obvious:

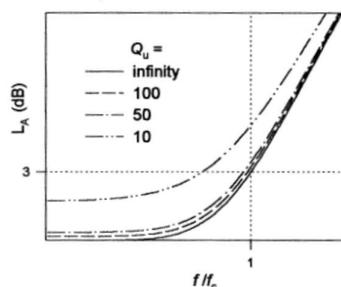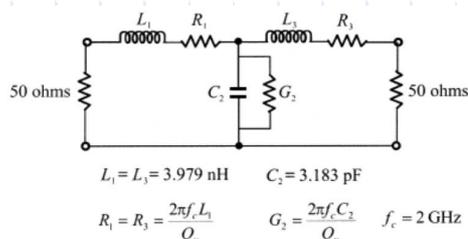1. A shift of insertion loss by a constant amount determined by the additional loss at zero frequency.
2. A gradual rounding off of the insertion loss curve at the passband edge, resulting in diminished width of the passband and hence in reduced selectivity.



The lowpass filter has used a  **$n = 3$  Butterworth lowpass prototype** with  $g_1 = g_3 = 1$ ,  $g_2 = 2$  and  $\Omega_c = 1$ . As assumed in the above example that  $Q_{u1} = Q_{u2} = Q_{u3} = Q_u$ , we then have  $\Delta L_{A0} = 0.174$  dB for  $Q_u = 100$ , and  $\Delta L_{A0} = 1.737$  dB for  $Q_u = 10$ , according to (3.61), which are in excellent agreement with the results obtained by network analysis.


Prof. T. L. Wu

## Dissipation Effect on Bandpass and Bandstop Filters


It should be mentioned that not only does the passband insertion loss increase and the selectivity become worse as the  $Q_u$  is decreased, but it also can be shown that for a given  $Q_u$ , the same tendencies occur as the fractional bandwidth of the filter is reduced.

$$\Delta L'_{A0} = 4.343 \sum_{i=1}^n \frac{\Omega_c}{FBW Q_{ui}} g_i \text{ dB}$$

The bandpass filter has a fractional bandwidth  $FBW = 0.707$  and a center frequency  $f_0 = 1.414$  GHz. Again, we assume that  $Q_{u1} = Q_{u2} = Q_{u3} = Q_u$ . Substituting these data into (3.62) yields  $\Delta L'_{A0} = 0.246$  dB for  $Q_u = 100$ , and  $\Delta L'_{A0} = 2.457$  dB for  $Q_u = 10$ , which are almost the same as those obtained by network analysis, as can be seen from Figure 3.31(b). The expression of

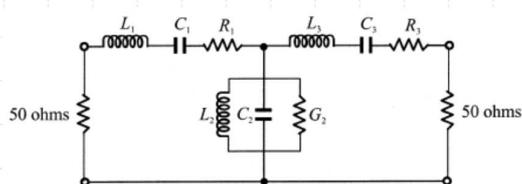
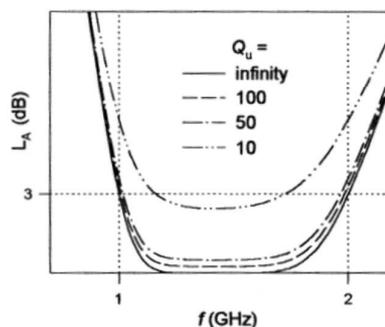
$$\begin{aligned} L_1 = L_3 &= 7.958 \text{ nH} & C_1 = C_3 &= 1.592 \text{ pF} \\ L_2 &= 1.989 \text{ nH} & C_2 &= 6.366 \text{ pF} \\ R_1 = R_3 &= \frac{2\pi f_0 L_1}{Q_u} & G_2 &= \frac{2\pi f_0 C_2}{Q_u} & f_0 &= 1.414 \text{ GHz} \end{aligned}$$



Prof. T. L. Wu

## HW #1

- ◆ Prove equation (3.24) for Butterworth Lowpass Prototype Filter
- ◆ Prove the equations shown in Fig. 3.18(a) and Fig. 3.18(b).
- ◆ Prove the equations shown in Fig. 3.19(a) and Fig. 3.19(b).
- ◆ Please prove the reactance slope parameters of a lumped LC series resonator is  $\omega_0 L$ , and the susceptance slope parameters of a lumped LC parallel resonator is  $\omega_0 C$ .
- ◆ Prove the equations shown in Fig. 3.20(a) and Fig. 3.20(b).
- ◆ Please prove Fig. 3.21(a) & (d) have a phase shift of +90 degree, and Fig. 3.21(b) & (c) have a phase shift of -90 degree.
- ◆ Please prove the identities in Fig. 3.27.